 



Introduction to yosys

Synthesizer


- Tool used for converting the RTL to netlist
- **Yosys** is the synthesizer used in this course



Yosys setup

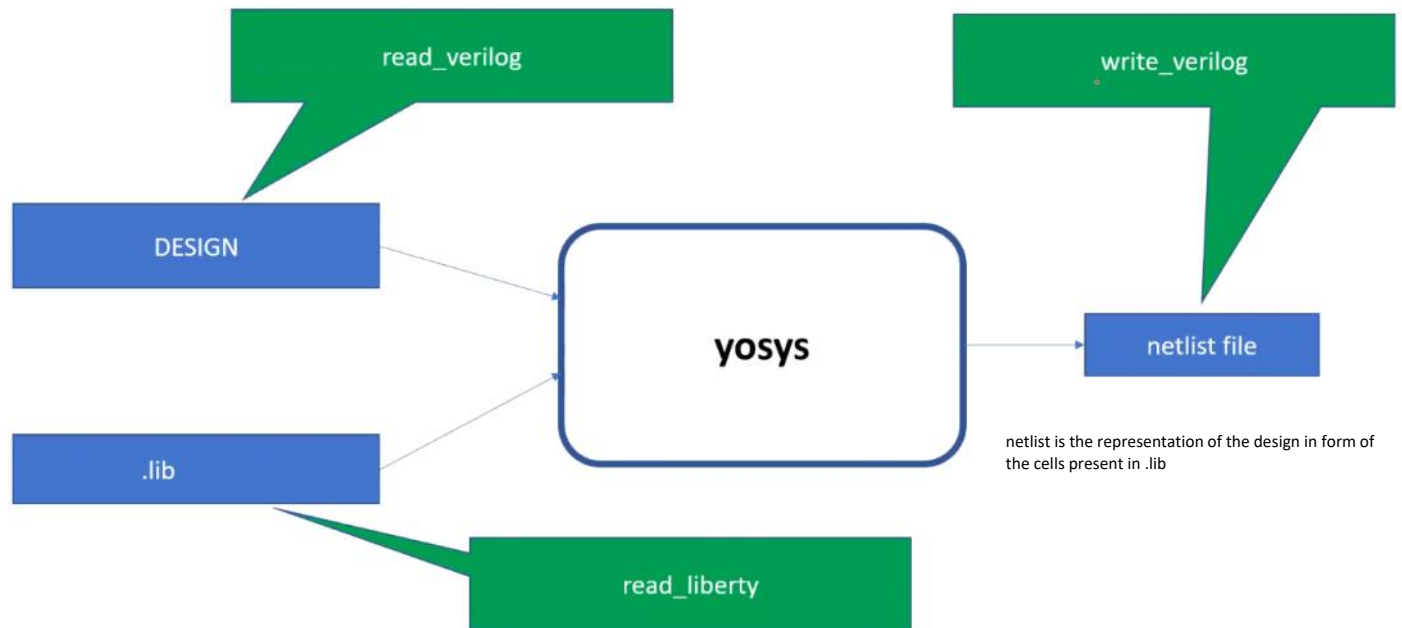

Verify the synthesis

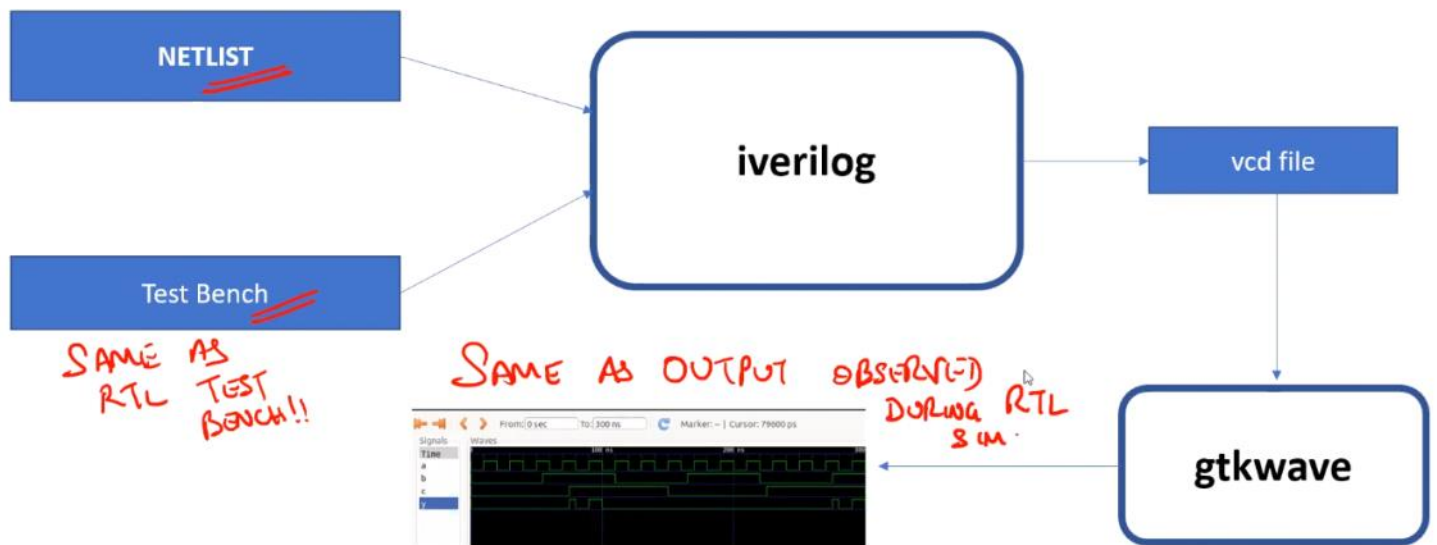

NOTE

The set of Primary inputs / primary outputs will remain same between the RTL design and Synthesized netlist → Same Test bench can be used !!

Logic Synthesis

RTL Design

- RTL Design
 - Behavioral representation of the required specification

```
module sample_code (  
  input clk,rst ,  
  output result,done);  
  
  always @ (posedge clk ,posedge rst)  
  if(rst)  
    ---  
  else  
    ---  
endmodule
```


VHDL
HDL

```

module sample_code (
input clk,rst ,
output result,done);

always @ (posedge clk ,posedge rst)
if(rst)
---
else
---
endmodule
-----
-----

```

 


Digital Logic Circuit

RTL CODE


Synthesis

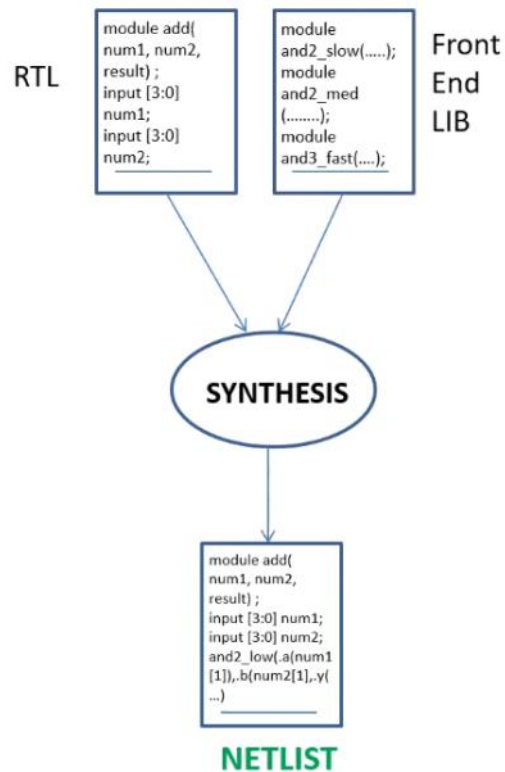- RTL to Gate level translation
- The design is converted into gates and the connections are made between the gates
- This is given out as a file called netlist




What is .lib

 - .lib
 - Collection of logical modules.
 - Includes basic logic gates like And, Or , Not, etc...
 - Different flavors of same gate
 - 2 input And gate
 - Slow
 - Medium
 - Fast
 - 3 input And gate
 - Slow
 - Medium
 - Fast
 - 4 input And gate
 - Slow
 - Medium
 - Fast
 -
 -



Why different flavours of gate

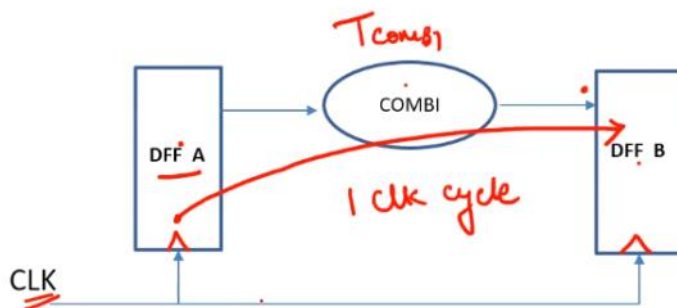- Combinational delay in logic path determines the maximum speed of operation of digital logic circuit



PROP. DELAY OF FLOP A

$$T_{CLK} > T_{CQ_A} + T_{COMBI} + T_{SETUP_B}$$

T_{clk}


$$f_{clk_max} = \frac{1}{T_{clk_min}}$$

- So we need cells that work fast to make T_{COMBI} small
- Are faster cells sufficient ?

$$T_{clk} \geq t_{pd1} + t_{comb} + t_{su2}$$


$$t_{h2} \leq t_{pd1} + t_{comb}$$

Why we need slow cells ?

 

- To ensure that there are no “HOLD” issues at DFF_B , we need cells that work slowly ☺ !!!
- Hence we need cells that work fast to meet the required performance and we need cells that work slow to meet HOLD
- The collection forms the lib

Faster Cells vs Slower Cells

 


- Load in Digital Logic circuit → Capacitance
- Faster the charging / discharging of capacitance → Lesser the cell delay

$$\beta = \mu C_{ox} \frac{W}{L} \quad I_{on} = \frac{\beta}{2} (V_{DD} - V_{th})^2 \quad W \uparrow, \beta \uparrow, I_{on} \uparrow, \text{delay} \downarrow$$
 - To charge / discharge the capacitance fast , we need transistors capable of sourcing more current → **WIDE TRANSISTORS**
 - Wider transistors -> Low Delay -> More Area and Power as well !!
 - Narrow transistors -> More Delay -> Less Area and Power
 - Faster cells donot come free , they come at penalty of area and power

Selection of Cells

- Need to guide the Synthesizer to select the flavour of cells that is optimum for the implementation of logic circuit
- More use of faster cells
 - Bad circuit interms of Power and Area
 - Hold time violations ??
- More use of slower cells
 - Sluggish circuit , may not meet the performance need
- The guidance offered to the Synthesizer → “Constraints”

Synthesis (Illustration)

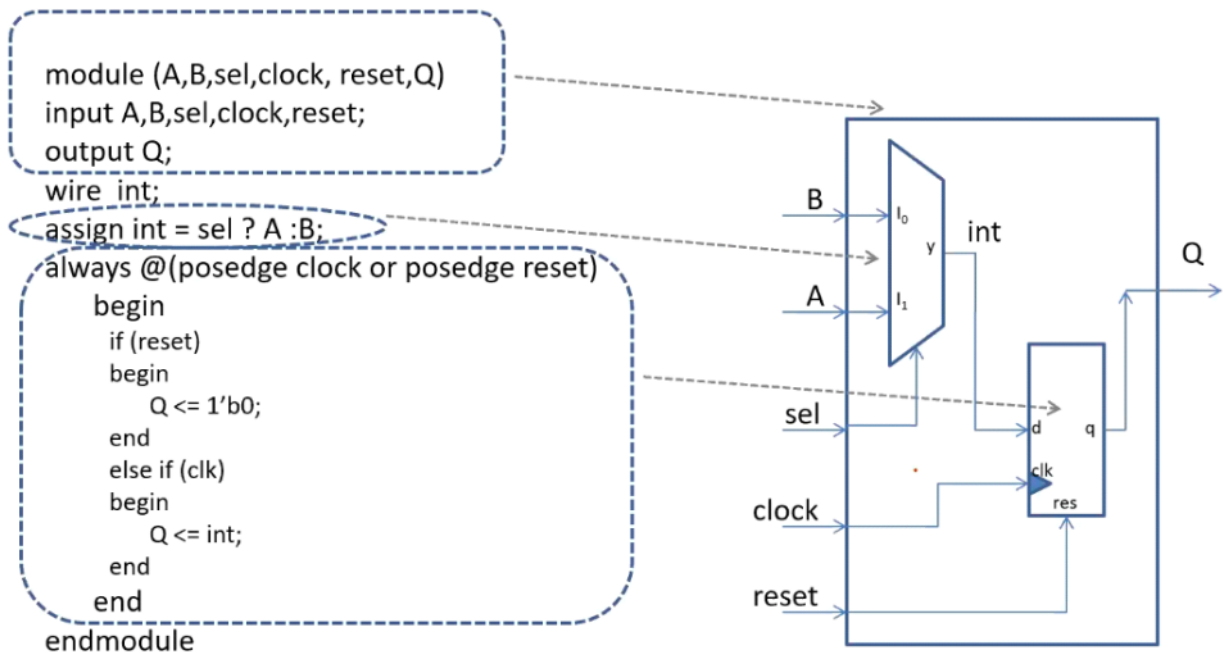

The circuit on the right is created from RTL using the gates available in the .Lib and given out as Netlist.